



Universidad Nacional Autónoma de México
Facultad de Ingeniería
Diseño Digital VLSI

Descripción de *hardware*

VHDL para circuitos secuenciales

M.I. Bryan Emmanuel Alvarez Serna






“Nadie puede hacerte sentir inferior sin tu consentimiento.”

Eleanor Roosevelt

► Introducción

► Asíncronos


► Síncronos

 


Circuitos secuenciales



Asíncrono

 

Síncrono

 


Contenido




► Introducción

► **Asíncronos**

► Síncronos

 

FFD

 


ENB	D	Q	Q'
1	1	1	0
1	0	0	1
0	1	Q	Q'
0	0	Q	Q'

ENB

D

Q

Q'

 

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;


ENTITY ffd IS
    PORT (ENB, D: IN STD_LOGIC;
          Q, QN: BUFFER STD_LOGIC);
END ENTITY;

ARCHITECTURE BEAS OF ffd IS
BEGIN

    PROCESS (ENB)
    BEGIN
        IF ENB = '1' THEN
            Q <= D; QN <= NOT(Q);
        ELSE
            Q <= Q; QN <= QN;
        END IF;
    END PROCESS;

END ARCHITECTURE;
```

ROM

 


```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
  
ENTITY rom IS  
  PORT (DIR: IN INTEGER RANGE 0 TO 3;  
         SAL: OUT STD_LOGIC_VECTOR(0 TO 7));  
END ENTITY;  
  
ARCHITECTURE BEAS OF rom IS  
  TYPE MEM IS ARRAY (0 TO 3) OF STD_LOGIC_VECTOR(0 TO 7);  
  CONSTANT ROM: MEM := ( X"F1", X"A8", X"9E", X"17");  
  BEGIN  
    SALIDA <= ROM(DIR);  
  END BEAS;
```

Contador asíncrono



 
Ejemplo: Contador asíncrono ascendente de 2 bits.



Contador asíncrono



 
Ejemplo: Contador asíncrono ascendente de 2 bits.



Contador asíncrono



 Ejemplo: Contador asíncrono ascendente de 2 bits.




¿Funciona?

Contador asíncrono



 
Ejemplo: Contador asíncrono ascendente de 2 bits.




¿Funciona?
No siempre...



Rebote

 

¿Cómo se soluciona?

 


Contenido




► Introducción

► Asíncronos

► Síncronos

 

Divisor de frecuencia

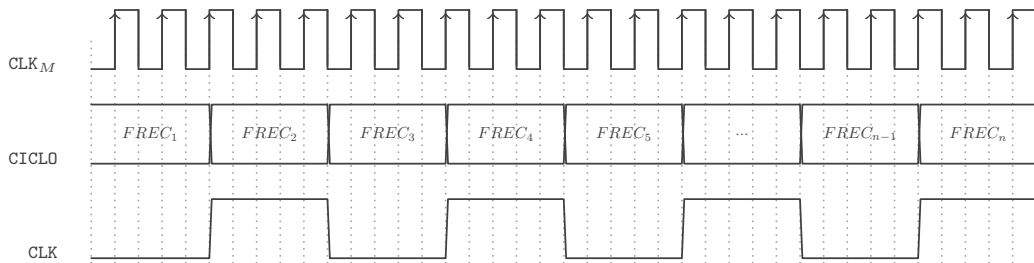

$$FREC = \frac{CLK_M}{2f_x} - 1$$

Divisor de frecuencia



```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY divisor IS
    GENERIC (FREC: INTEGER := 24999999); -- FREC = (50 MHz/2*Fdeseada) - 1
        -- 24999    >> 1 kHz
        -- 249999   >> 100 Hz
        -- 24999999 >> 1 Hz
    PORT (CLK_MST: IN STD_LOGIC; -- RELOJ PRINCIPAL
          CLK: BUFFER STD_LOGIC);
END ENTITY;

ARCHITECTURE BEAS OF divisor IS
    SIGNAL AUX: INTEGER RANGE 0 TO FREC;
BEGIN

    PROCESS (CLK_MST)
    BEGIN
        IF RISING_EDGE (CLK_MST) THEN
            IF AUX = 0 THEN
                CLK <= NOT CLK;
                AUX <= FREC;
            ELSE
                AUX <= AUX - 1;
            END IF;
        END IF;
    END PROCESS;

END BEAS;
```


Contador síncrono



Ejemplo: Contador síncrono de anillo de n bits.



Contador síncrono




Ejemplo: Contador síncrono de anillo de n bits con RST o PRST.




RST y PRST



RST: Reiniciar.

 

PRST: Preestablecer.

 

Contador con RST



```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY conta IS
PORT (CLK, RST: IN STD_LOGIC;
      CUENTA: BUFFER INTEGER RANGE 0 TO 7);
END ENTITY;

ARCHITECTURE BEAS OF conta IS
BEGIN
  PROCESS (CLK, RST)
  BEGIN
    IF RST = '1' THEN
      CUENTA <= 0;
    ELSIF FALLING_EDGE (CLK) THEN
      IF CUENTA = 7 THEN
        CUENTA <= 0;
      ELSE
        CUENTA <= CUENTA + 1;
      END IF;
    END IF;
  END PROCESS;
END BEAS;
```

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;


ENTITY conta IS
PORT (CLK, RST: IN STD_LOGIC;
      CUENTA: BUFFER INTEGER RANGE 0 TO 7);
END ENTITY;

ARCHITECTURE BEAS OF conta IS
BEGIN
  PROCESS (CLK, RST)
  BEGIN
    IF FALLING_EDGE (CLK) THEN
      IF RST = '1' THEN
        CUENTA <= 0;
      ELSIF CUENTA = 7 THEN
        CUENTA <= 0;
      ELSE
        CUENTA <= CUENTA + 1;
      END IF;
    END IF;
  END PROCESS;
END BEAS;
```


Contador con RST




Contador con RST síncrono

 

Contador con RST asíncrono

 

Contador con HAB

 

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY conta IS
PORT(CLK, HAB: IN STD_LOGIC;
      CUENTA: BUFFER INTEGER RANGE 0 TO 7);
END ENTITY;

ARCHITECTURE BEAS OF conta IS
BEGIN
  PROCESS(CLK, HAB)
  BEGIN
    IF FALLING_EDGE(CLK) THEN
      IF HAB = '1' THEN
        CUENTA <= CUENTA;
      ELSIF CUENTA = 7 THEN
        CUENTA <= 0;
      ELSE
        CUENTA <= CUENTA + 1;
      END IF;
    END IF;
  END PROCESS;
END BEAS;
```

Contador con carga paralela





```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY conta IS
PORT(CLK, HAB: IN STD_LOGIC;
      CARGA: IN INTEGER RANGE 0 TO 7;
      CUENTA: BUFFER INTEGER RANGE 0 TO 7);
END ENTITY;

ARCHITECTURE BEAS OF conta IS
BEGIN
  PROCESS(CLK, HAB)
  BEGIN
    IF FALLING_EDGE(CLK) THEN
      IF CUENTA = CARGA THEN
        CUENTA <= 0;
      ELSE
        CUENTA <= CUENTA + 1;
      END IF;
    END IF;
  END PROCESS;
END BEAS;
```

Contador por década

  

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;


ENTITY contadec IS
    PORT (CLK: IN STD_LOGIC;
          D, U: BUFFER INTEGER RANGE 0 TO 9);
END ENTITY;

ARCHITECTURE BEAS OF contadec IS
BEGIN

    PROCESS (CLK)
    BEGIN
        IF FALLING_EDGE (CLK) THEN
            IF U = 9 THEN
                U <= 0;
                IF D = 9 THEN
                    D <= 0;
                ELSE
                    D <= D + 1;
                END IF;
            ELSE
                U <= U + 1;
            END IF;
        END IF;
    END PROCESS;

END BEAS;
```


Contador con MOD

 

Ejemplo:

$25/20 = 2$ y sobran 5

$\therefore 25 \text{ MOD } 10 = 5$

$(25/10) \text{ MOD } 10 = 2.5$

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

ENTITY contamod IS
    PORT(CLK: IN STD_LOGIC;
          D, U: OUT INTEGER RANGE 0 TO 9);
END ENTITY;

ARCHITECTURE BEAS OF contamod IS
    SIGNAL CUENTA: INTEGER RANGE 0 TO 99;
BEGIN


    PROCESS(CLK)
    BEGIN
        IF FALLING_EDGE(CLK) THEN
            IF CUENTA = 99 THEN
                CUENTA <= 0;
            ELSE
                CUENTA <= CUENTA + 1;
            END IF;
        END IF;
    END PROCESS;

    PROCESS(CUENTA)
    BEGIN
        U <= CUENTA MOD 10;
        D <= (CUENTA/10) MOD 10;
    END PROCESS;
```


Comparación de hardware






Por década

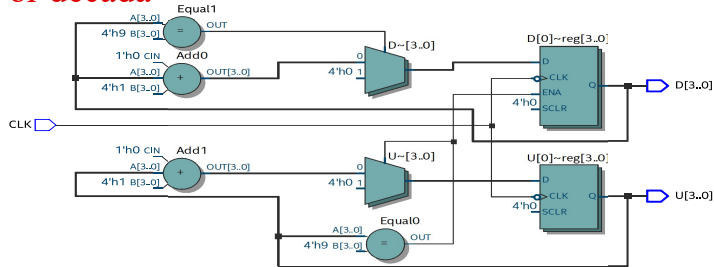


Con MOD

 

Registro SIPO

   

Registro SIPO

 

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;


ENTITY reg_d IS
    PORT (NUM: IN INTEGER RANGE 0 TO 9;
          CLK: IN STD_LOGIC;
          Q1,Q2,Q3: BUFFER INTEGER RANGE 0 TO 9);
END ENTITY;

ARCHITECTURE BEAS OF reg_d IS
BEGIN

    PROCESS (CLK)
    BEGIN
        IF RISING_EDGE (CLK) THEN
            Q1 <= NUM;
            Q2 <= Q1;
            Q3 <= Q2;
        END IF;
    END PROCESS;

END BEAS;
```

Memoria RAM

 

```
ENTITY ram IS
    PORT (CLK, RW: STD_LOGIC;
          DIR: IN INTEGER RANGE 0 TO 7;
          SAL: OUT INTEGER RANGE 0 TO 255;
          DATO: IN INTEGER RANGE 0 TO 255);
END ENTITY;

ARCHITECTURE BEAS OF ram IS
    TYPE MEMORIA IS ARRAY (0 TO 7) OF INTEGER RANGE 0 TO 255;
    SIGNAL RAM: MEMORIA;
    BEGIN
        PROCESS (CLK)
        BEGIN
            IF RISING_EDGE (CLK) THEN
                IF RW = '1' THEN
                    RAM(DIR) <= DATO;
                ELSE
                    SAL <= RAM(DIR);
                END IF;
            END IF;
        END PROCESS;
    END BEAS;
```